


## Part I

$$f = xs' + ys$$

We could express the above Boolean function using logic words :

$$f = (x \text{ AND (NOT } s) \text{) OR (} y \text{ AND } s \text{)}$$

 1. Draw the gate diagram that implements this 2-to-1 multiplexer design.



2. Write out the truth table for this design.

$x$	$s$	$y$	$xs'$	$ys$	$f$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	0	1	1


## Part II

$$f = (a + b)' + cb'$$

We could express the above Boolean function using logic words :

$$f = (\text{NOT}(a \text{ OR } b)) \text{ OR } (c \text{ AND } (\text{NOT } b))$$

 1. Draw the gate diagram for the function shown above.



2. Write out the truth table for this expression.


$a$	$b$	$c$	$(a+b)'$	$cb'$	$f$
0	0	0	1	0	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	0	0	0
1	1	1	0	0	0

3. Yes, there is a cheaper implementation for the design that uses fewer gates.

$$\begin{aligned} f &= (a + b)' + cb' \\ &= a'b' + cb' \quad \text{by De Morgan's Law} \\ &= b'(a' + c) \end{aligned}$$

which in logic words:  $f = (\text{NOT } b) \text{ AND } ((\text{NOT } a) \text{ OR } c)$

 ① Draw the gate diagram for the function shown above.




② Write out the truth table for this expression.

a	b	c	b'	a'+c	f
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	0	1	0

### Part III

 1. Implemented circuit from Part I and its test result screenshots.




Test Vector main of Lab1\_PartI

Passed: 8 Failed: 0

Status	x	s	y	f
pass	0	0	0	0
pass	0	0	1	0
pass	0	1	0	0
pass	0	1	1	1
pass	1	0	0	1
pass	1	0	1	1
pass	1	1	0	0
pass	1	1	1	1

Load Vector Run Stop Reset Close Window

 2. Implemented circuit from Part II and its test result screenshots.



Test Vector main of Lab1\_PartII

Passed: 8 Failed: 0

Status	a	b	c	f
pass	0	0	0	1
pass	0	0	1	1
pass	0	1	0	0
pass	0	1	1	0
pass	1	0	0	0
pass	1	0	1	1
pass	1	1	0	0
pass	1	1	1	0

Load Vector Run Stop Reset Close Window